


The background of the slide features two decorative, jagged, sawtooth-like lines in a dark gray color. One line starts from the left edge and curves upwards towards the bottom right. The other line starts from the top right edge and curves downwards towards the bottom right. These lines frame the central text area.

HOW SERVOS WORK



JUSTIN SELIG

ECE 3400


9-21-2017

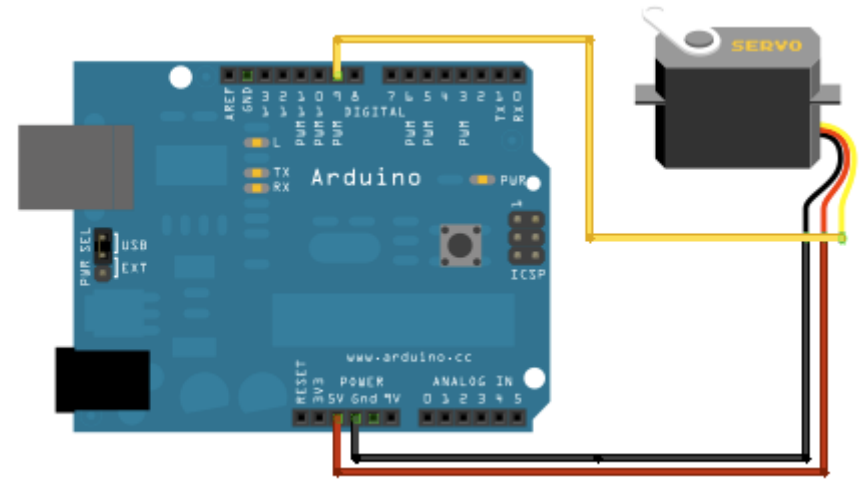

Positional | Continuous

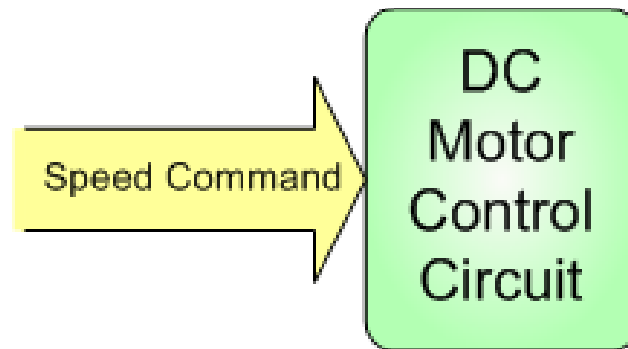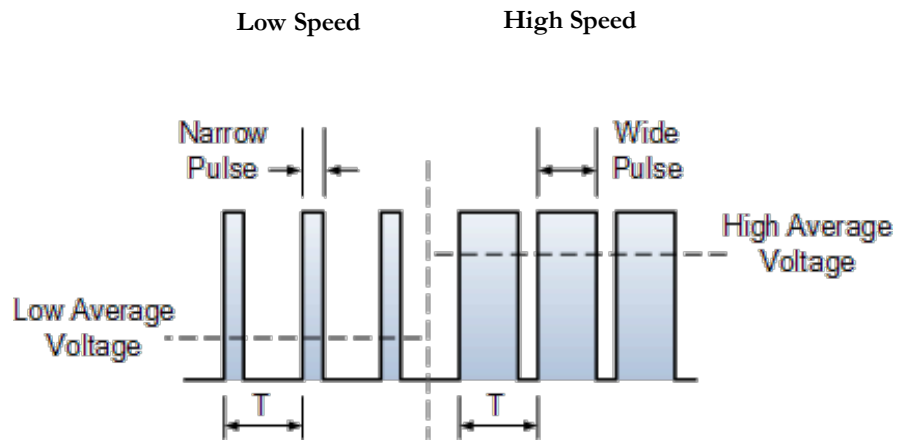

Continuous

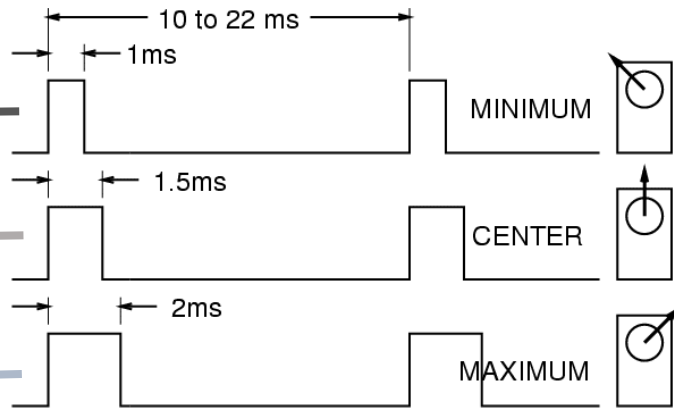


Arduino Code:

`myservo.write(0)`

`myservo.write(90)`


`myservo.write(180)`

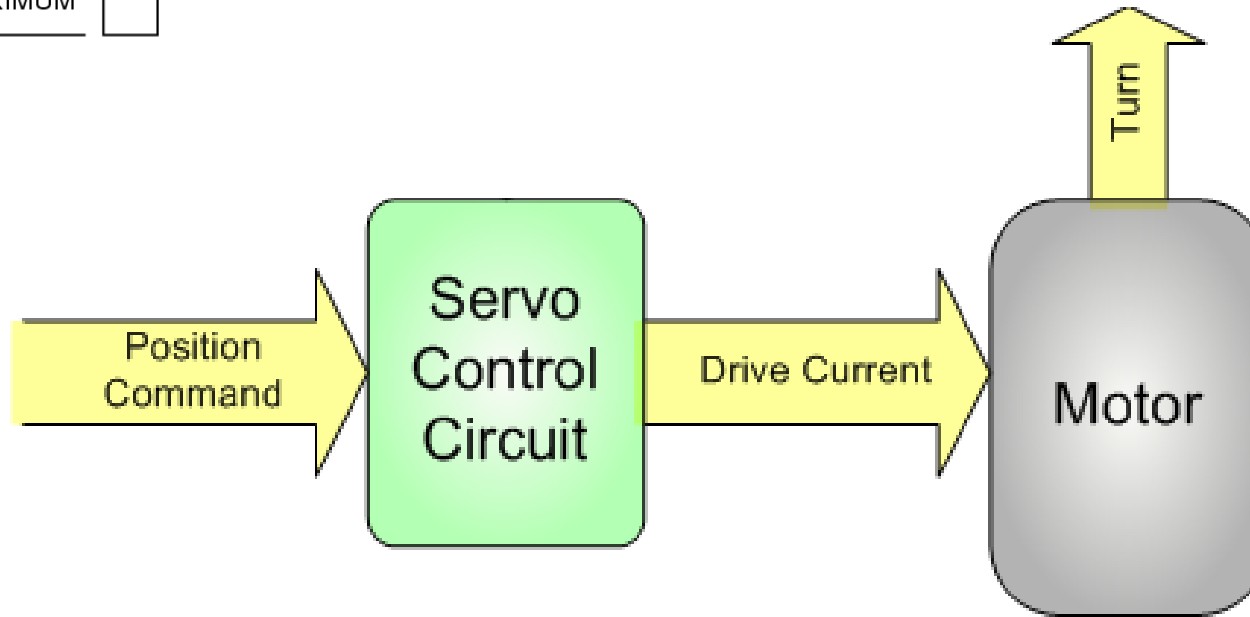

Positional






Positional | Continuous

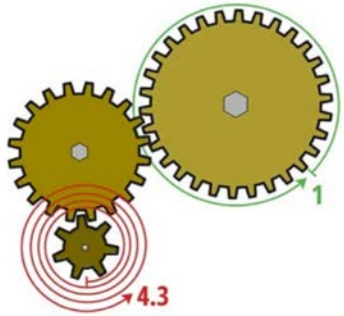

$$v_3 = v_1 \cdot \frac{N_1}{N_3}$$
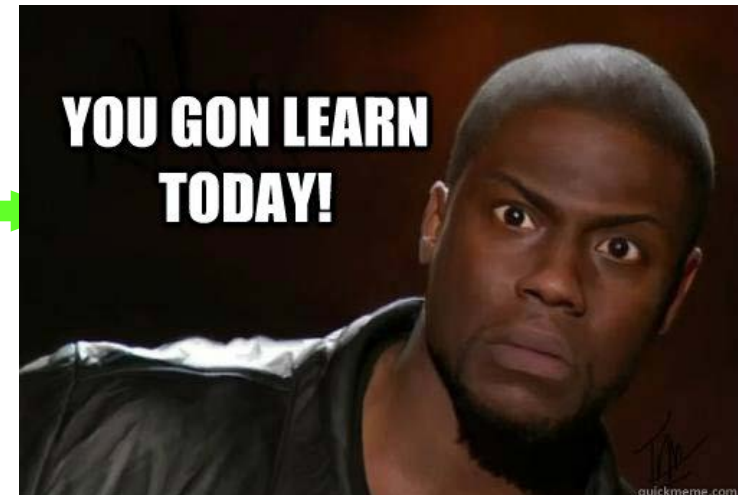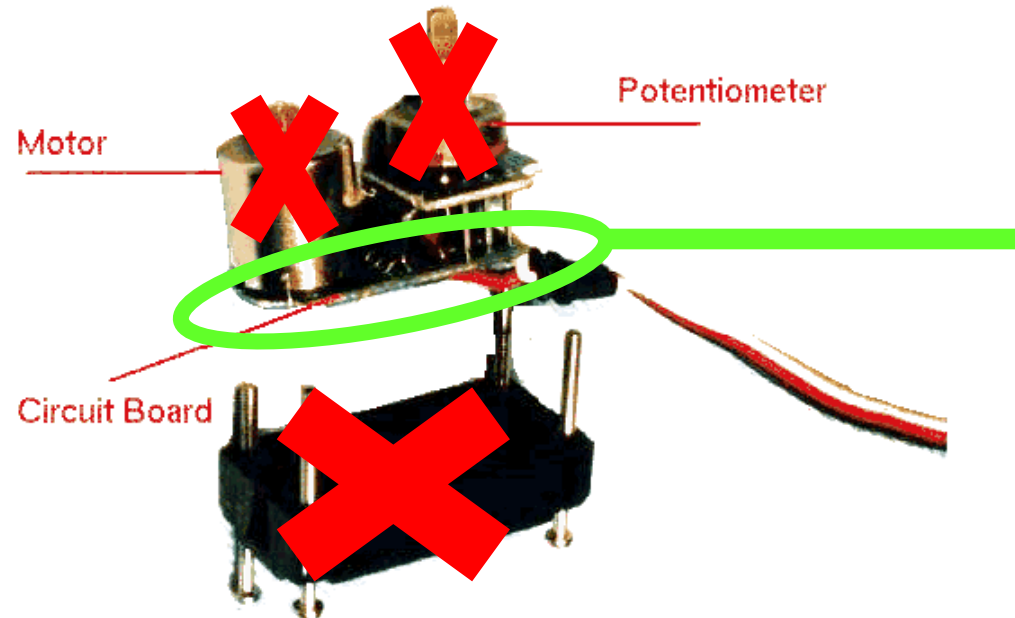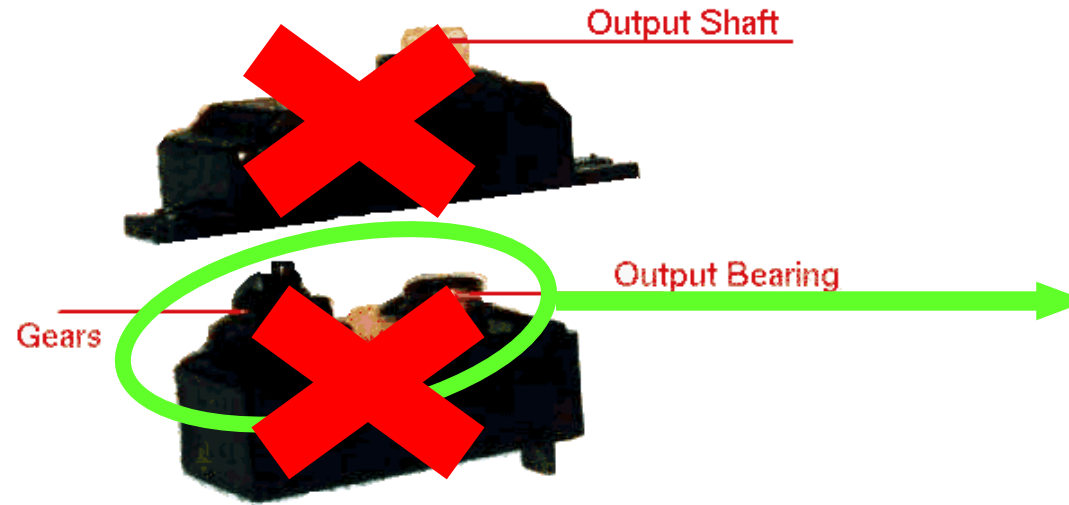
$$v_3 = v_1 \cdot \frac{N_1}{N_2} \cdot \frac{N_2}{N_3}$$




Positional | Continuous


Let's Take it Apart!

Futaba S3003 Circuit Changes


Figure 1

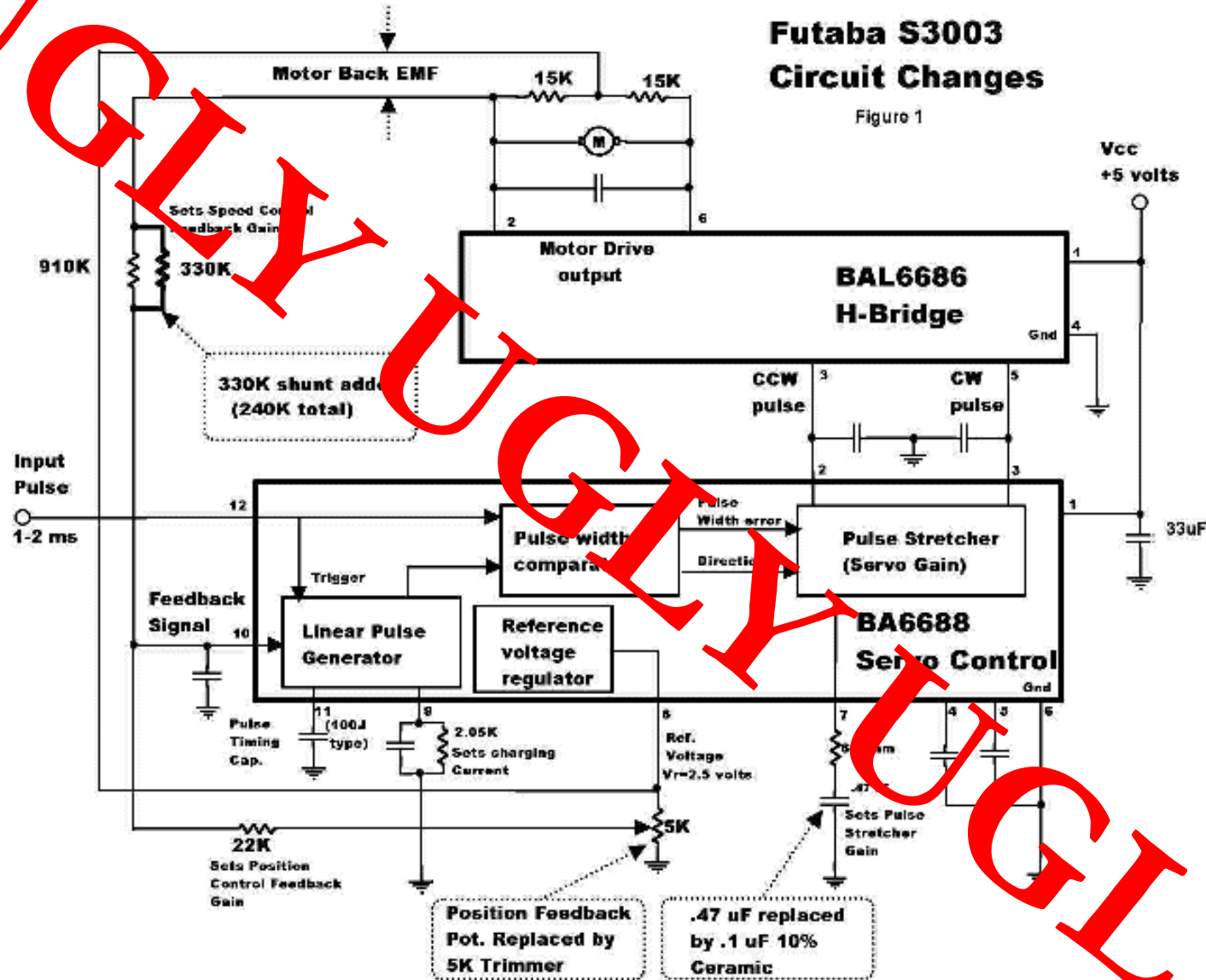


1) How do you control a motor?

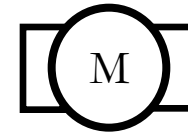


2) What are inputs to an H-Bridge?

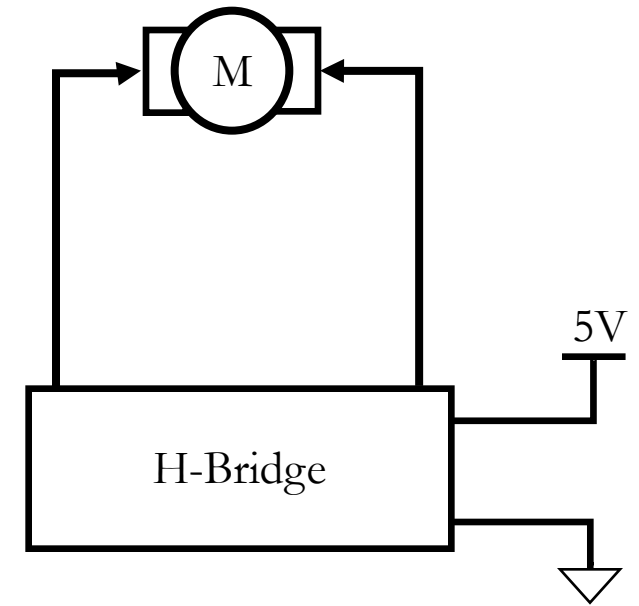


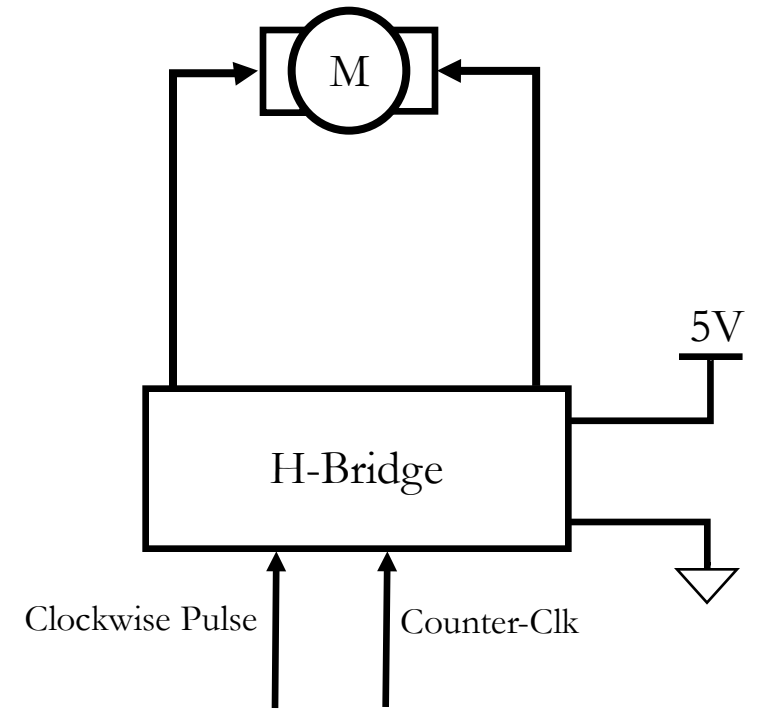
3) What's providing input to the H-Bridge?



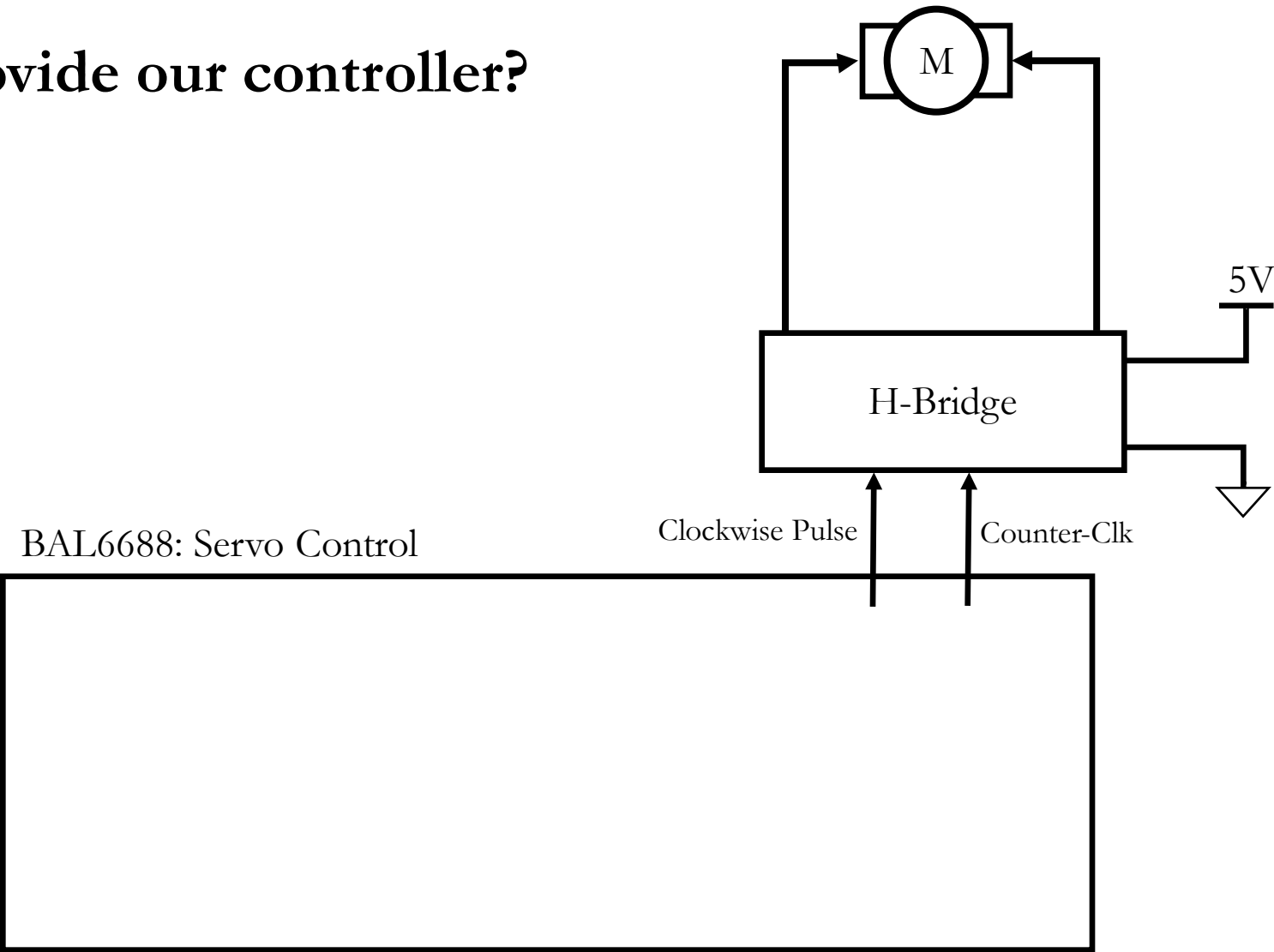
4) What input to we provide our controller?



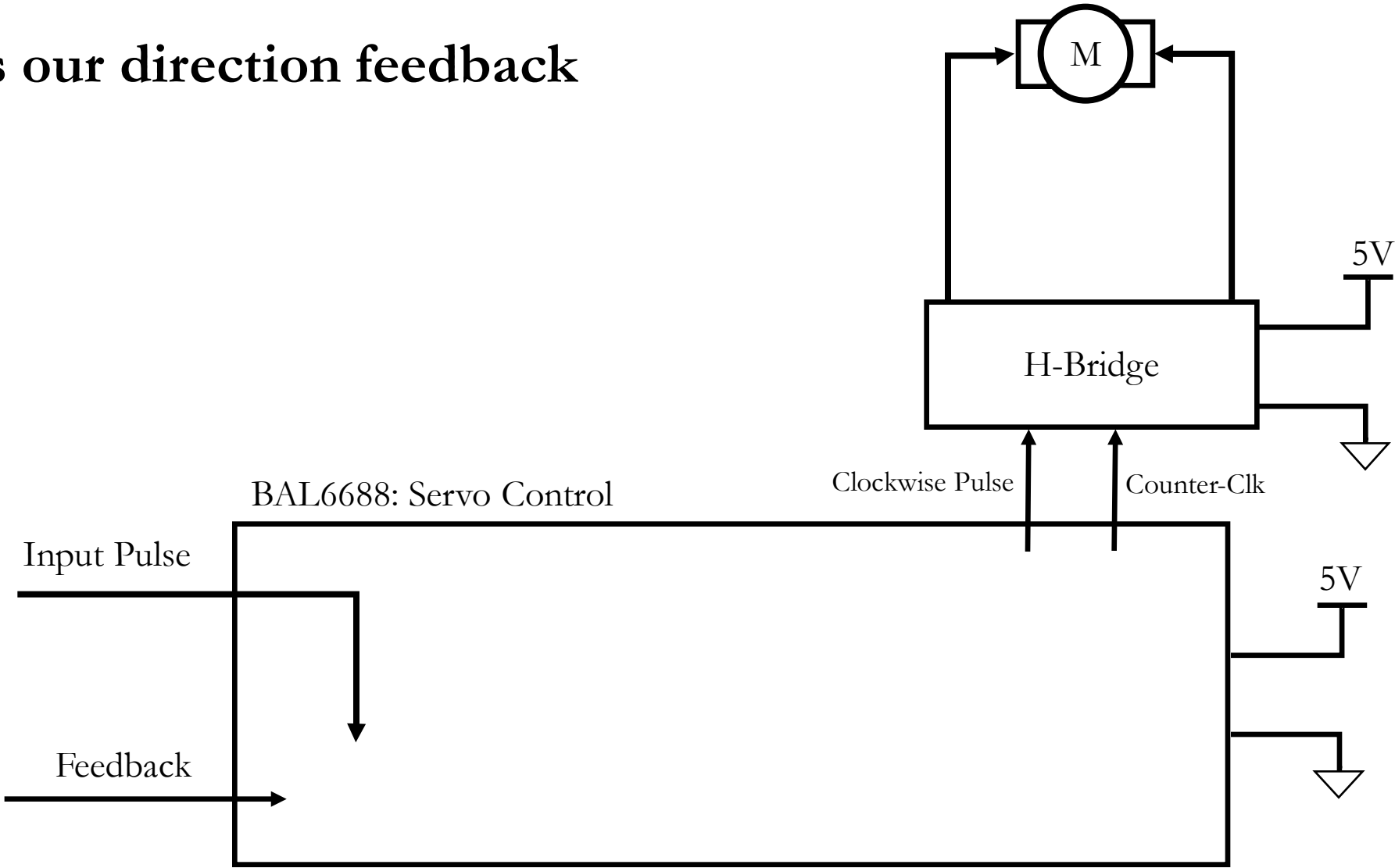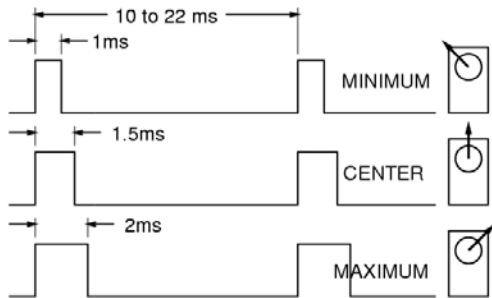
5) Where does our direction feedback come from?



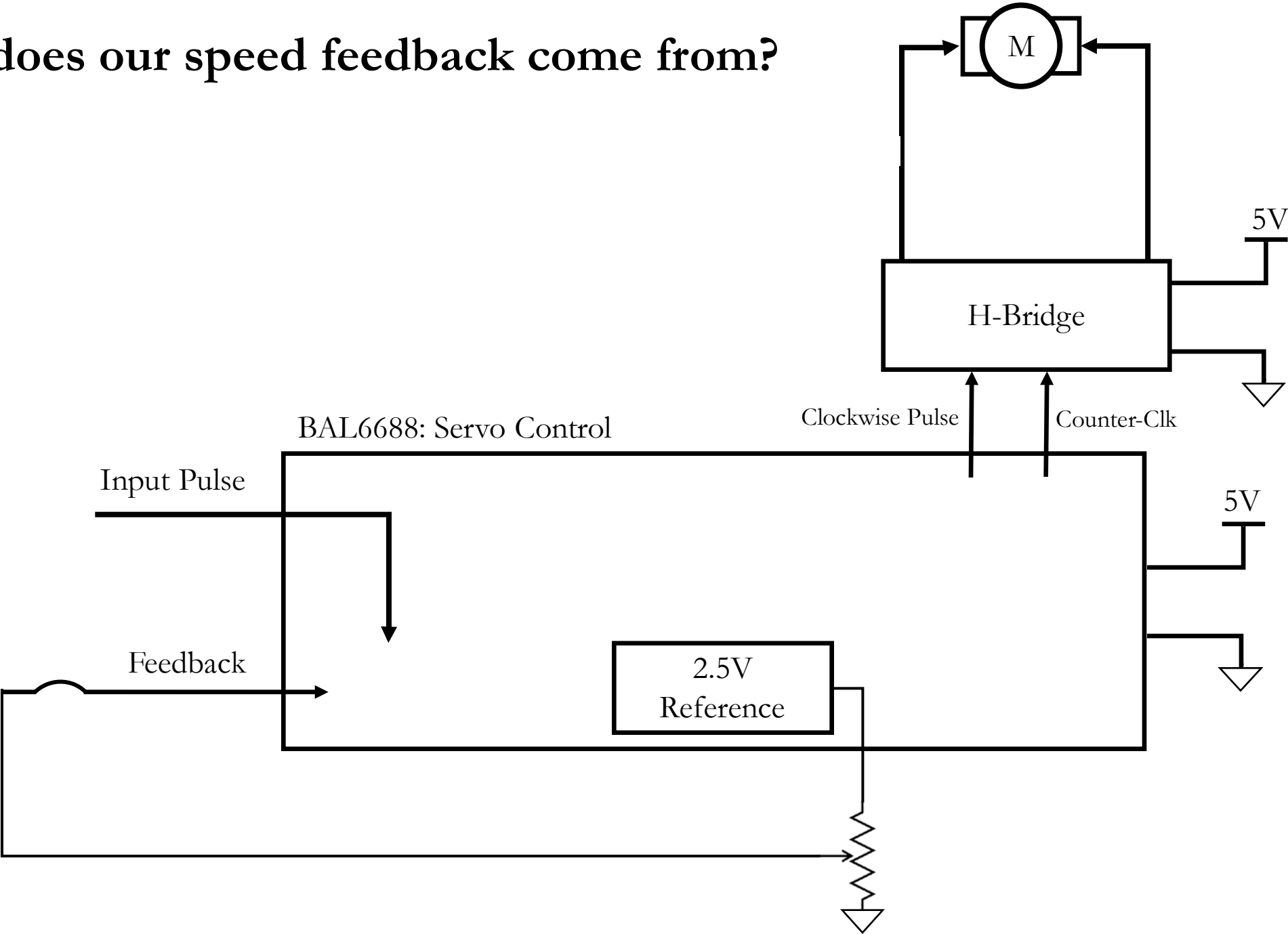
6) Where does our speed feedback come from?




7) What now?

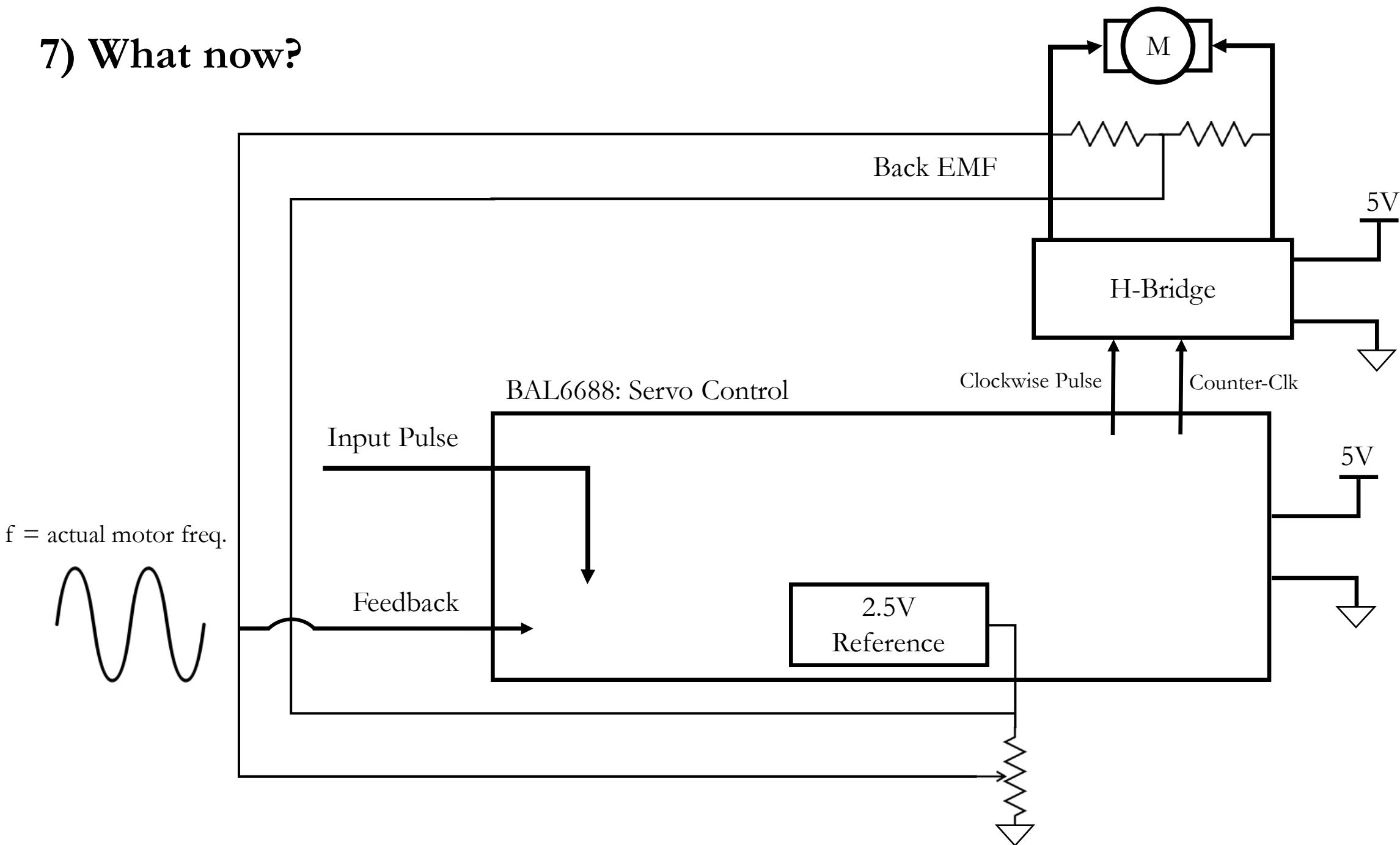

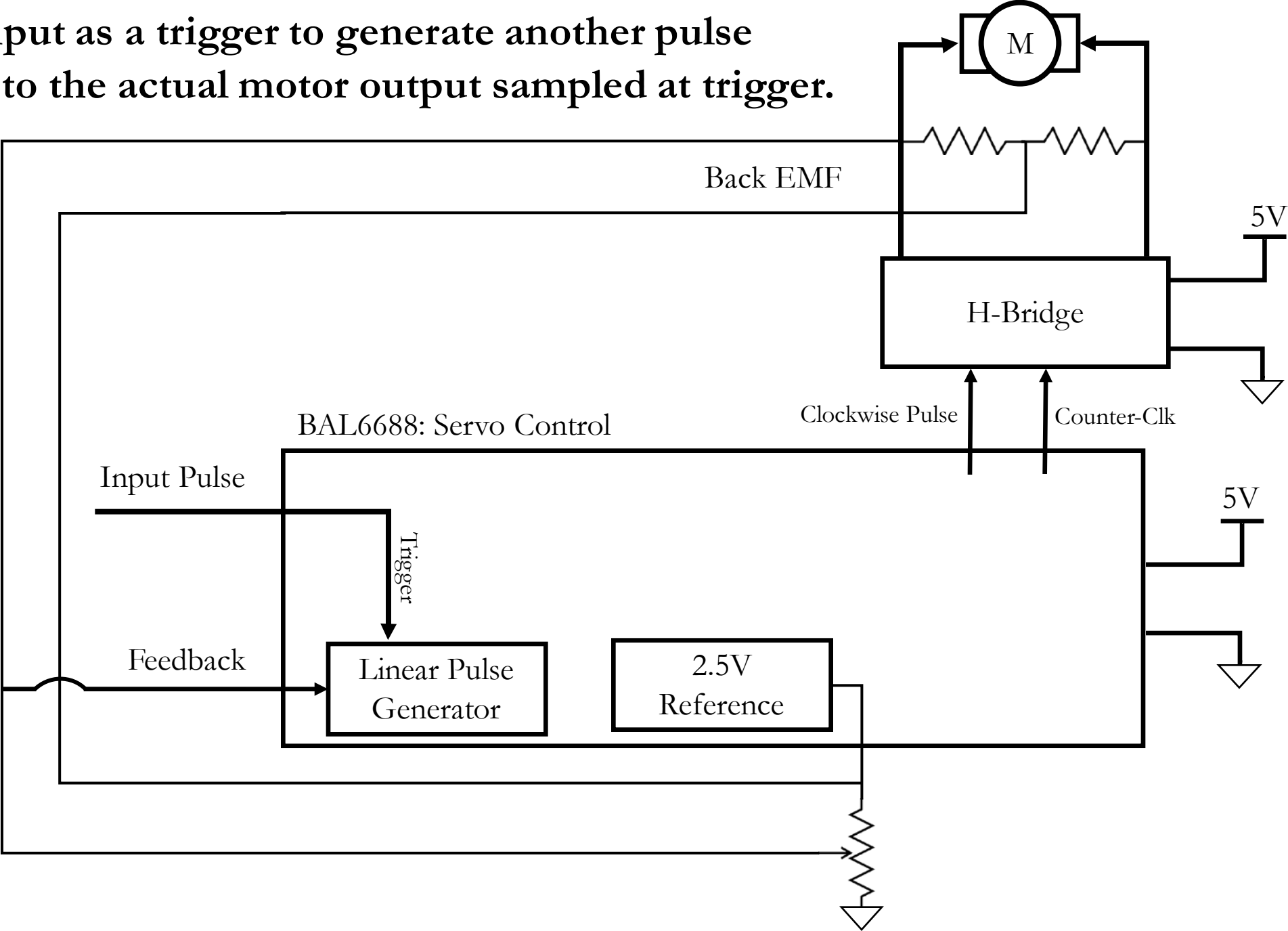
8) Use our input as a trigger to generate another pulse proportional to the actual motor output sampled at trigger.



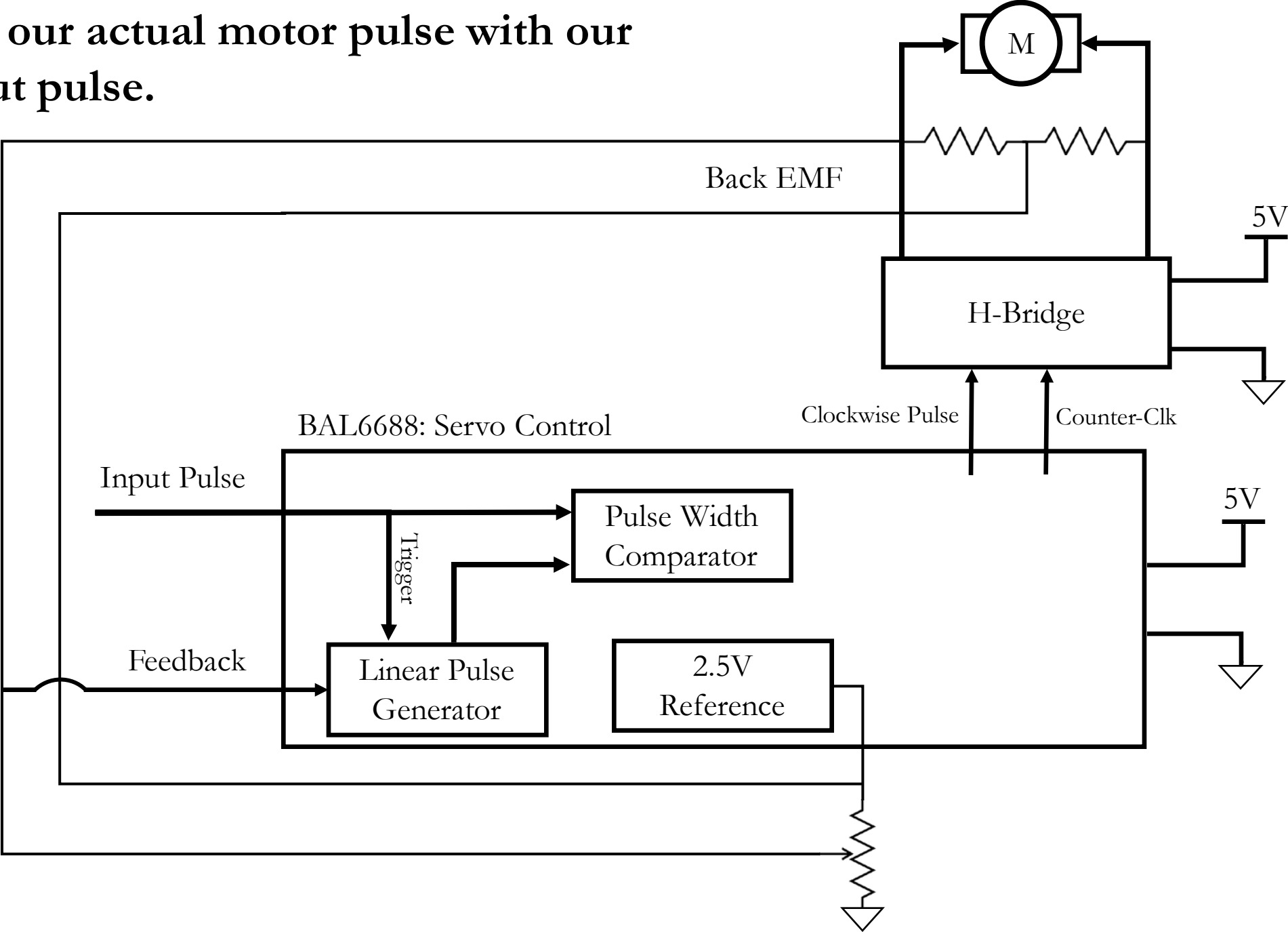
9) Compare our actual motor pulse with our desired input pulse.



10) Derive an error and direction term.

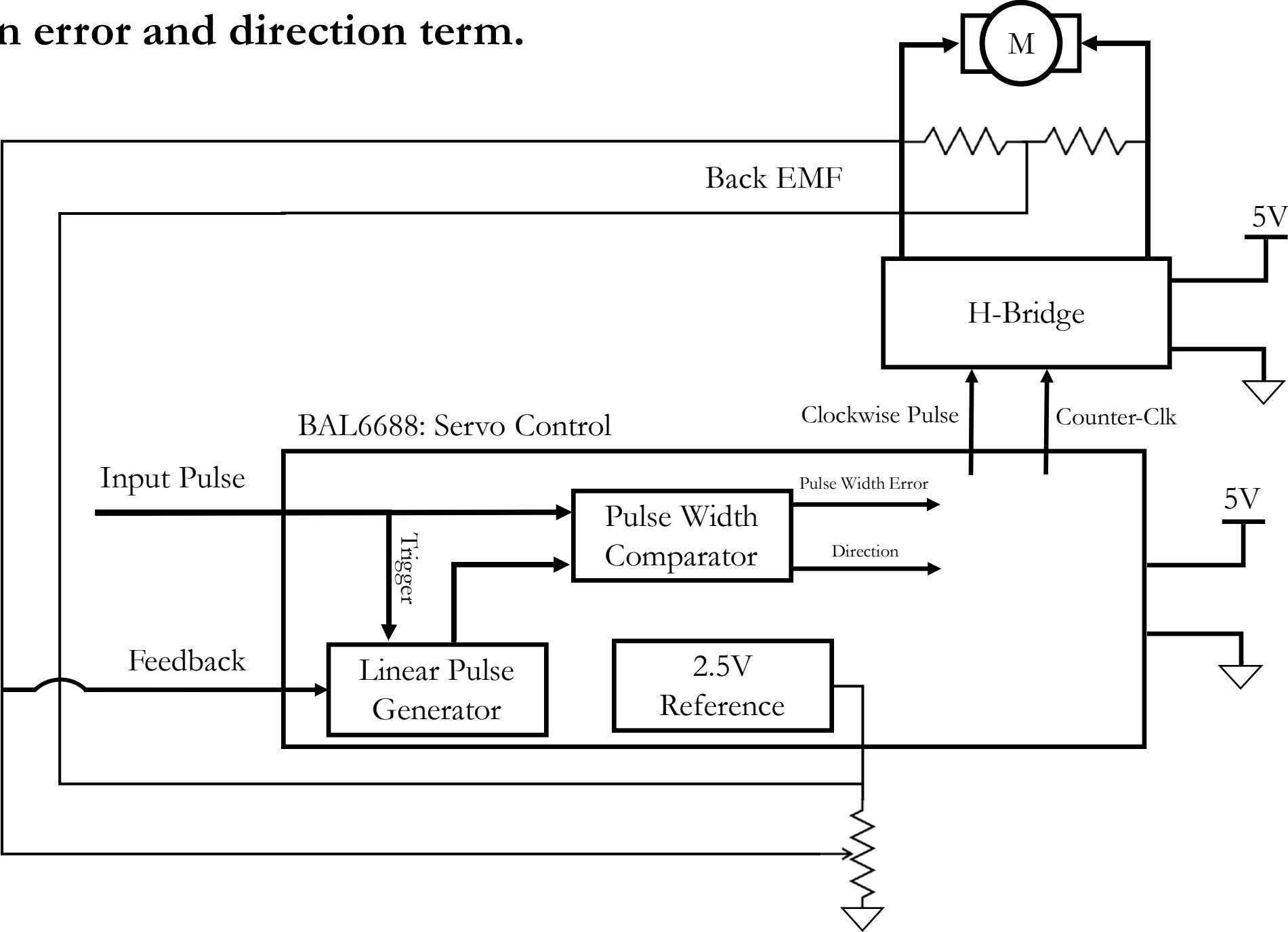


11) Generate H-Bridge signals.

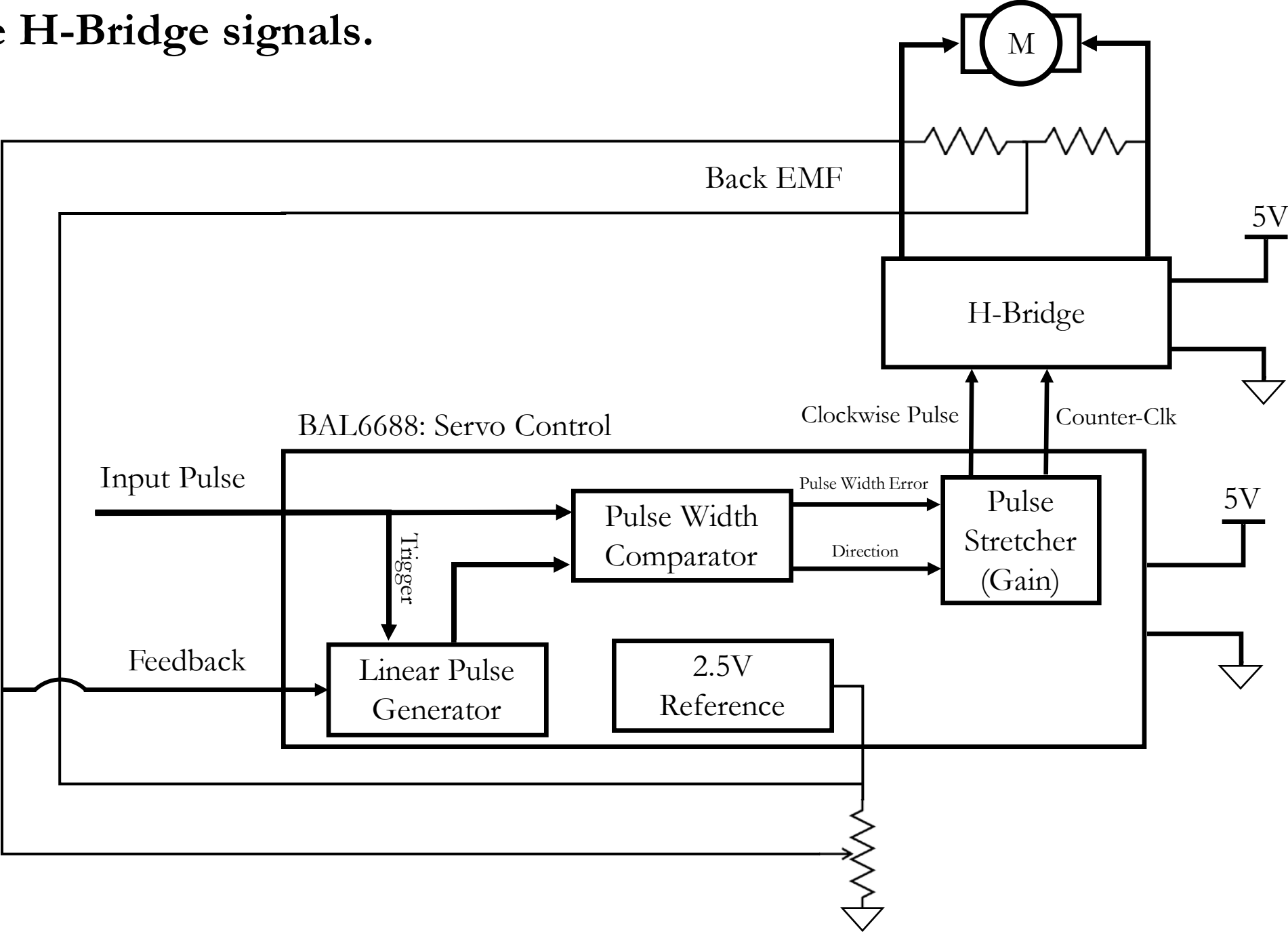


Futaba S3003 Circuit Changes

Figure 1

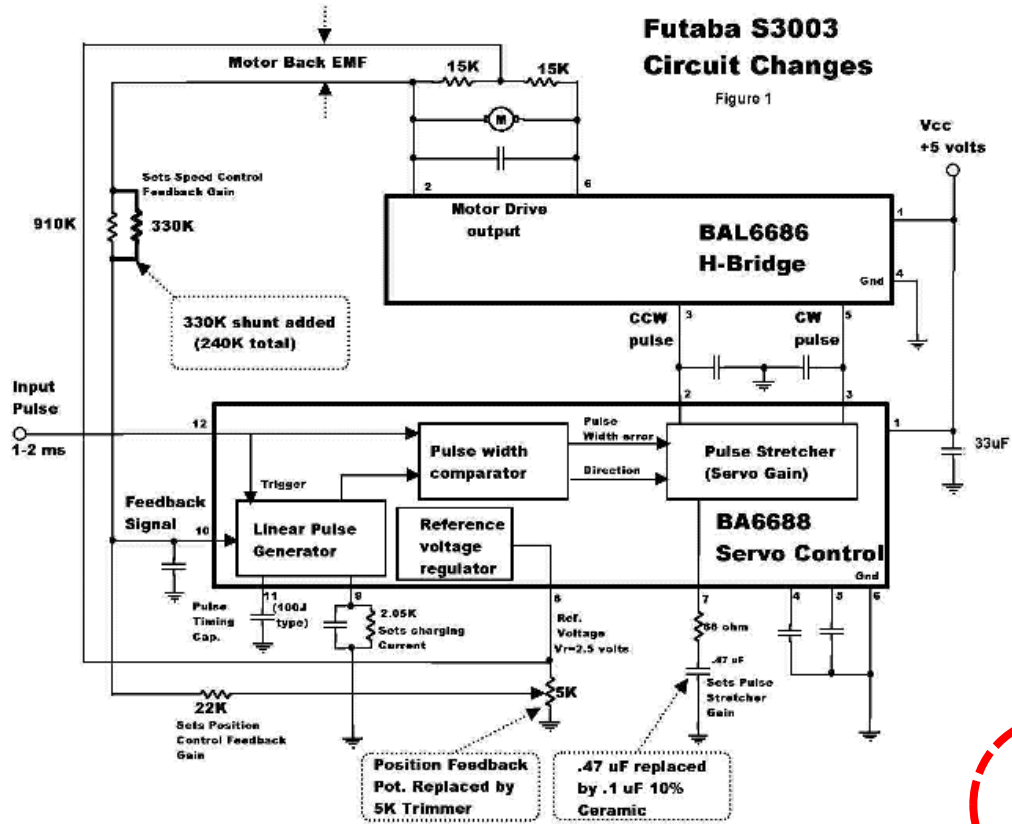

L. Buse
8/15/00

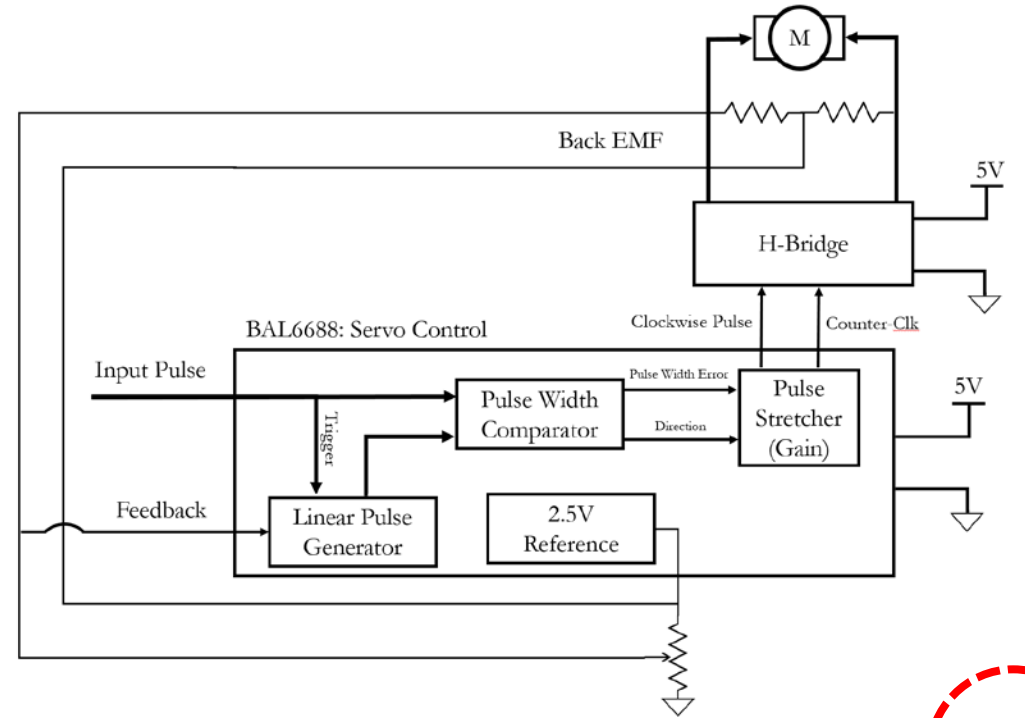

J. Selig
9/22/17



MAKE ROBOTS!

JUSTIN SELIG
JSS459@CORNELL.EDU
JUSTIN-SELIG.COM